

Design and Analysis of a Two-Stage CMOS Operational Transconductance Amplifier

Rishav

1 Introduction

This project walks through the process of building and analyzing the performance of a **Two-Stage Unbuffered CMOS Operational Transconductance Amplifier (OTA)** using SPICE.

It is done to teach myself how to design circuits rather than simply analyze the equations or solve problems in standard college curricula.

1.1 Why a two-stage CMOS OTA?

The two stage CMOS OTA is an introductory circuit in the study of op-amps that uses a standard single output differential pair and a common source stage in cascade, making it easier to analyze.

- It uses cascaded topology which provides higher gain compared to single stage amplifiers.
- The second stage uses only 2 transistors, which results in high output swing.
- CMOS amps suffer less from non-idealities compared to their BJT counterparts due to their extremely high input impedance.


The above reasons make it a very enticing circuit to learn design process without getting overwhelmed.

2 Architecture and Topology

The two-stage op-amp consists of a differential amplifier converting the differential input voltage to differential currents. These differential currents are applied to a current-mirror load recovering the differential voltage. This is nothing but a differential amplifier.

The second stage consists of common-source MOSFET converting the second-stage input voltage into current. This transistor is loaded by a current-sink load, which converts the current to voltage at the output.

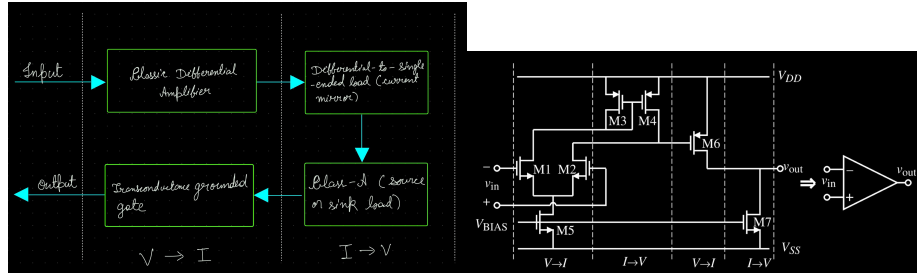The block diagram and transistor-level broken into $V \rightarrow I$ and $I \rightarrow V$ stages is shown in Fig 1.



(a) Block diagram of $V \rightarrow I$ and $I \rightarrow V$ stages (b) Transistor level diagram. Adapted from (Allen and Holberg 2011)

Figure 1: Architecture of the two-stage OTA.

3 Theoretical Design and Calculations

The design of op-amps can be divided into two distinct design related activities that are for the most part independent of each other.

- The general schematic, which we have already decided above.
- Calculating the DC currents, sizing up the transistors and designing the compensation network, based on the requirements.

The boundary conditions and requirements we will need to design our op-amp:

- Boundary Conditions:
 1. Process Specification (V_T , K' , C_{ox} , etc.)
 2. Supply Voltage and Range
- Requirements:
 1. Gain
 2. Unity Gain Bandwidth
 3. Slew Rate
 4. Input Common-Mode range ($ICMR$)
 5. Output-voltage swing
 6. Phase Margin
 7. Power Dissipation

In our first iteration, let us use the basic topology shown in Fig 2.

The small signal model for this circuit is shown in Fig 3.

The locations of the two poles are given as:

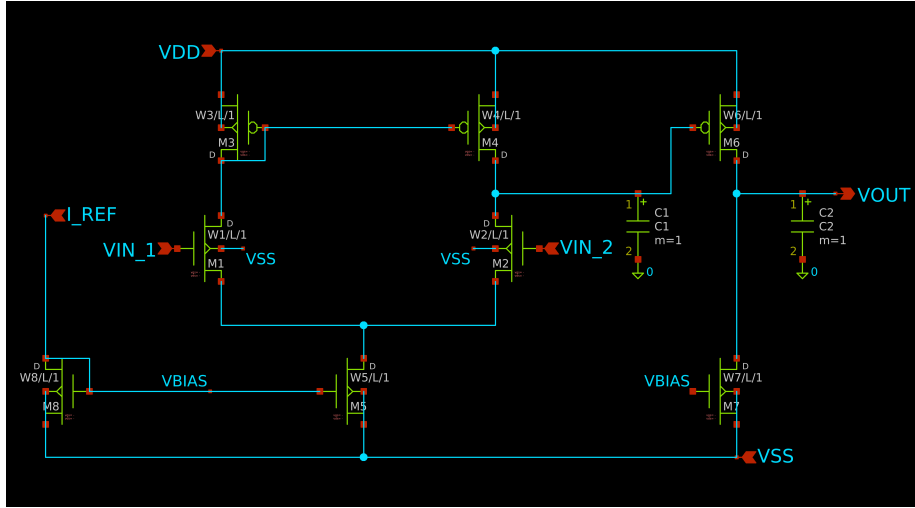


Figure 2: Uncompensated Two-Stage CMOS OTA

 


Figure 3: Small Signal model of the uncompensated OTA

$$p'_1 = \left(\frac{-1}{R_I \cdot C_I}\right)$$

and,

$$p'_2 = \left(\frac{-1}{R_{II} \cdot C_{II}}\right)$$

Where R_I/C_I and R_{II}/C_{II} are resistance/capacitance to ground seen from the output of the first stage and second stage respectively.

In most cases, these poles are far away from the origin and relatively close together. Fig 4 illustrates the open-loop frequency response of the negative-feedback loop op-amp in Fig 2.

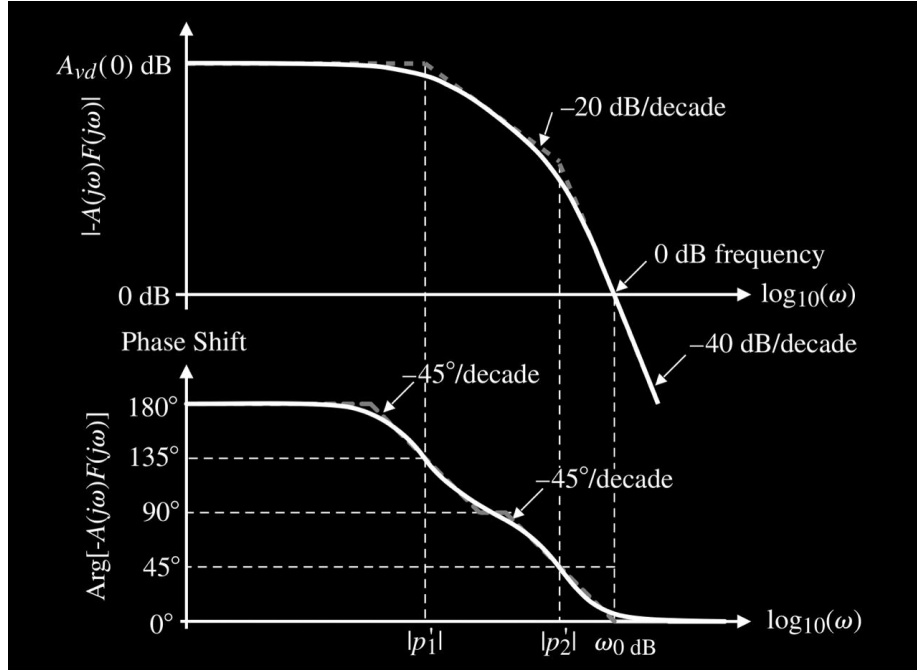


Figure 4: Open-Loop frequency response of negative-feedback loop of an uncompensated op-amp. Adapted from (Allen and Holberg 2011)

As seen in Fig 4, the phase margin is significantly less than 45° , which will lead to instability. Thus, the op-amp needs to be compensated before using it in a closed loop configuration.

3.1 Miller Compensation

Adding the compensation capacitor C_c , the resulting circuit is shown in Fig 5:

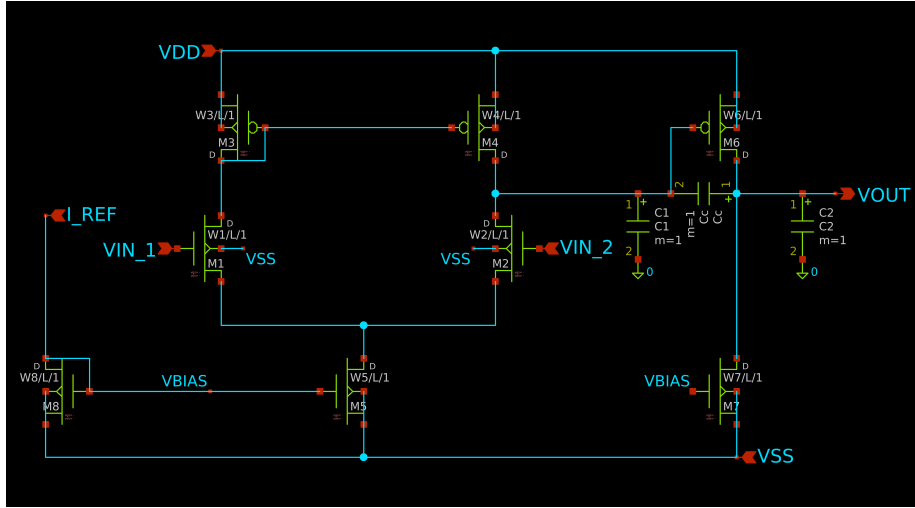


Figure 5: Compensated Two-Stage op-amp

 


Figure 6: Small-signal model of the compensated two-stage op-amp. Adapted from (Allen and Holberg 2011)

The resulting small-signal model is shown in Fig 6:

Using Miller's Approximation and finding poles by inspection, we get

$$p_1 \approx \left(\frac{-1}{R_I \cdot [C_I + C_c(1 + g_{mII} \cdot R_{II})]} \right)$$

and,

$$p_2 \approx \left(\frac{-g_{mII}}{C_{II} + C_c} \right) \approx \left(\frac{-g_{mII}}{C_{II}} \right); \text{ if } C_{II} > C_c$$

A zero also occurs on the positive real axis, which can be found from the small signal model relatively easily by setting $A_v = 0$

$$z_1 = \left(\frac{g_{mII}}{C_c} \right)$$

The addition of miller capacitance moves the dominant pole (p_1) to the left and shifts the non dominant pole (p_2) to the right.

If we use our assumption of $C_{II} > C_c$, then the zero is further to the right of (p_2)

Fig 7 shows results of compensation compared to the uncompensated state.

The **Unity Gain Bandwidth** is defined as the angular frequency (or frequency) when the gain crosses the 0dB mark. It is given as:

$$(\omega_{GBW}) \approx \left(\frac{g_{mI}}{C_c} \right)$$

If we define $z_1 > 10 \cdot \omega_{GBW}$, then, to achieve $\phi_M > 60^\circ$, we need the following condition:

$$p_2 > 2.2 \cdot \omega_{GBW}$$

OR,

$$C_c > 0.22 \cdot C_2$$

3.2 Component Sizing

Before beginning, let us summarise the important relationships:

1. First Stage Gain:

$$A_{v1} = \frac{-g_{m1}}{g_{ds2} + g_{ds4}} = \frac{-2 \cdot g_{m1}}{I_5 \cdot (\lambda_2 + \lambda_4)}$$

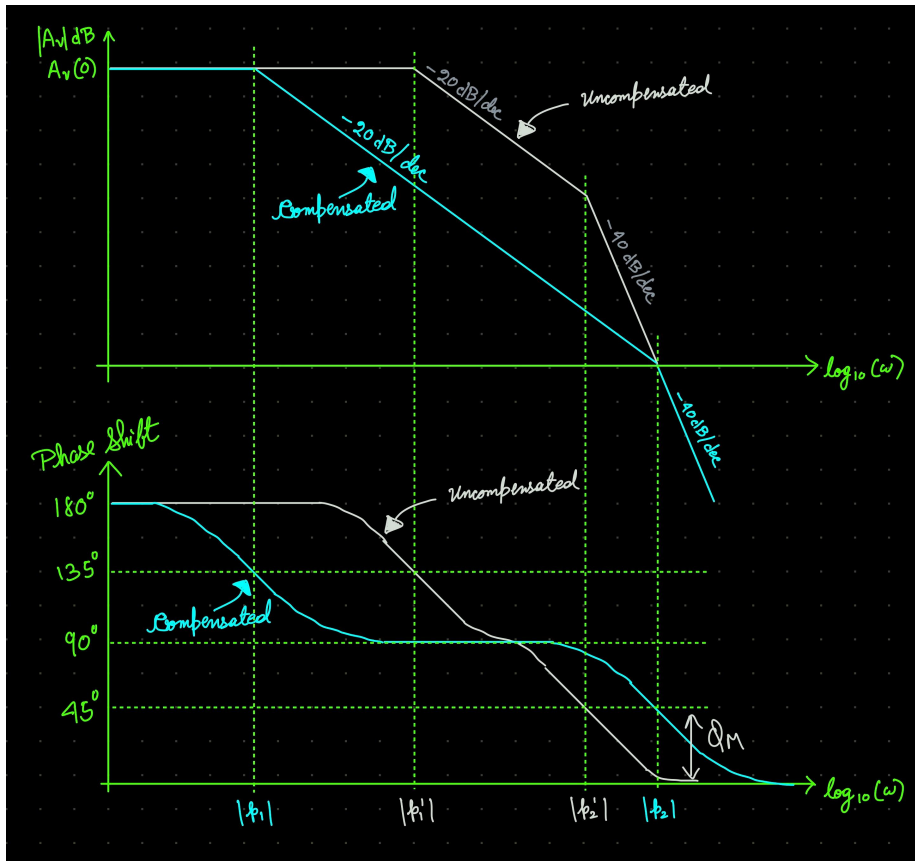


Figure 7: Position of Poles and Zeroes in Compensated and Uncompensated OTA

2. Second Stage Gain:

$$A_{v2} = \frac{-g_{m6}}{g_{ds6} + g_{ds7}} = \frac{-2 \cdot g_{m6}}{I_6 \cdot (\lambda_6 + \lambda_7)}$$

3. Unity Gain Bandwidth:

$$\omega_{GBW} \approx \frac{g_{m2}}{C_c}$$

4. Slew Rate:

$$SR = \frac{I_5}{C_c}$$

5. $ICMR_{max} = V_{in}(max) =$

$$V_{DD} - \sqrt{\frac{I_5}{K'(\frac{W}{L})_3}} - |V_{T03}(max) + V_{T1}(min)|$$

6. $ICMR_{min} = V_{in}(min) =$

$$V_{SS} + \sqrt{\frac{I_5}{K'(\frac{W}{L})_1}} + V_{T1}(max) + V_{DS5}(sat)$$

7. Saturation Voltage:

$$V_{DS5}(sat) = \sqrt{\frac{2 \cdot I_{DS}}{K'(\frac{W}{L})}}$$

Going onto the design procedure, a first cut sequence we can follow is:

- The design procedure begins by choosing a device length to be used by the circuit. This length determines the channel length modulation parameter (λ), which is necessary to calculate amplifier gain.
- Keeping our definition of $z_1 > 10 \cdot \omega_{GBW}$, minimum value of C_c can be defined as:

$$C_c > 0.22 \cdot C_2$$

- Next, minimum value of tail current (I_5) can be determined by :

$$I_5 = SR \cdot C_c$$

- The aspect ratio of M3 can now be determined using $ICMR_{max}$ as:

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = \frac{I_5}{(K'_3) \cdot (ICMR_{max})^2}$$

- Requirement of transconductance of input transistors can be determined from the knowledge of C_c and f_{GBW}

$$g_{m1} = g_{m2} = \omega_{GBW} \cdot C_c$$

- The aspect ratio of the input transistors are directly obtainable from g_{m1} as:

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{g_{m1}^2}{K'_1 \cdot I_5}$$

- The saturation voltage of M5 can now be calculated using $ICMR_{min}$

$$V_{DS5} = (ICMR_{min}) - V_{SS} - \sqrt{\frac{I_5}{K' \left(\frac{W}{L}\right)_1}} - V_{T1}(max)$$

- With V_{DS5} determined, the aspect ratio of M5 can be extracted as:

$$\left(\frac{W}{L}\right)_5 = \frac{2 \cdot I_5}{K'_5 \cdot (V_{DS5})^2}$$

- Again, following $z_1 > 10 \cdot \omega_{GBW}$, we can calculate the transconductance of M6 as:

$$g_{m6} = 2.2(g_{m2}) \left(\frac{C_L}{C_c}\right)$$

- To achieve proper current mirroring of first-stage current mirror load, $V_{SG4} = V_{SG6}$. using $g_m = K' \cdot \left(\frac{W}{L}\right) (V_{GS} - V_T)$

$$\left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_4 \cdot \left(\frac{g_{m6}}{g_{m4}}\right)$$

- Knowing g_{m6} and $\left(\frac{W}{L}\right)_6$, we can determine current flowing through M6 as:

$$I_6 = \frac{g_{m6}^2}{2 \cdot K'_6 \cdot \left(\frac{W}{L}\right)_6}$$

- Aspect ratio of M7 can be extracted from the balancing equation below:

$$\left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_5 \cdot \left(\frac{I_6}{I_5}\right)$$

- We calculate power dissipated as the *total current flowing through the supply voltage * total supply voltage*

$$P_{dis} = (I_5 + I_6 + I_8) \cdot (V_{DD} + |V_{SS}|)$$

- Now, the gain must be checked against the specifications. If it is too low, I_5 and I_6 may be decreased or the ratios $\left(\frac{W}{L}\right)_2$ and $\left(\frac{W}{L}\right)_6$ may be increased. All the previous calculations need to be performed again to ensure all conditions are satisfied.

3.3 Biasing Network

- A current mirror approach with a stable reference current source (say, using $\beta - Multiplier$) is used to bias the current sink M_7 and tail current source M_5
 - Since M_8 acts as our reference current mirror, we can have $(\frac{W}{L})_8 = (\frac{W}{L})_5$ to set $I_{tail} = I_{ref}$, and the relation of $(\frac{W}{L})_5$ with $(\frac{W}{L})_7$ is known from above calculations.
- The Bias Point of the differential input is found as:

$$g_m = \frac{2I_D}{V_{ov}} \implies |A_{v1}| = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{2}{V_{ov} \cdot (\lambda_2 + \lambda_4)} \implies V_{ov} = \frac{2}{|A_{v1}| \cdot (\lambda_2 + \lambda_4)}$$

3.4 Requirements and Specifications

The specifications we will use are as follows:

$$\begin{aligned} A_v &> 5000V/V \\ f_{GBW} &= 5MHz \\ \phi_M &> 60^\circ \\ ICMR_{min} &= -1V \\ ICMR_{max} &= 2V \\ SR &> 10V/\mu s \\ V_{out} &\pm 2V \\ V_{DD} &= 2.5V \\ V_{SS} &= -2.5V \\ C_L &= 10pF \\ P_{dis} &< 2mW \\ L &= 1\mu m \end{aligned}$$

The important process parameters from the model used are:

$$\begin{aligned} K'_n &= 120\mu A/V^2 \\ V_{TN} &= 0.8V \\ \lambda_n &= 0.04V^{-1}(atL = 1\mu m) \\ K'_p &= 40\mu A/V^2 \\ V_{TP} &= -0.9V \\ \lambda_p &= 0.05V^{-1}(atL = 1\mu m) \end{aligned}$$

3.5 Initial Sizing

Following the design procedure and substituting the values from requirements and process parameters, the initial calculated values are:

$$C_c = 3pF$$

$$I_5 = 30\mu A$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 \approx 10$$

$$g_{m1} = g_{m2} = 94.2\mu S$$

$$g_{m3} = g_{m4} = 109\mu S$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 \approx 3$$

$$V_{DS5}(sat) = 0.411V$$

$$\left(\frac{W}{L}\right)_5 \approx 3$$

$$g_{m6} = 942\mu S$$

$$\left(\frac{W}{L}\right)_6 \approx 86.6$$

$$I_6 = 130\mu A$$

$$\left(\frac{W}{L}\right)_7 \approx 13$$

$$V_{CM} = 1.118V$$

$$A_v \approx 5600V/V$$

$$P_{dis} = 0.95mW$$

These initial values were entered into **xschem** and simulated. The following sections document the schematic implementation, challenges encountered in measuring the open-loop gain and the iterative refinements made to meet all specifications.

Parameter	Calculated Value	Specification
-----------	------------------	---------------

3.6 Pre-Simulation Results

Based on the napkin math above, the following performance is expected:

Parameter	Calculated Value	Specification
DC Gain	$\approx 74.9dB(5600V/V)$	$> 73.98dB(5000V/V)$
GBW	$5MHz$	$5MHz$
Phase Margin	66.03°	$> 60^\circ$
Slew Rate	$10V/\mu s$	$> 10V/\mu s$
Power	$0.95mW$	$< 2mW$

3.7 Schematic Implementation

The circuit was implemented in Xschem and simulated using the Ngspice engine, utilizing a Level 3 SPICE model(Baker, n.d.-b) for a $1\mu m$ CMOS process. The complete schematic is shown in Fig 8.

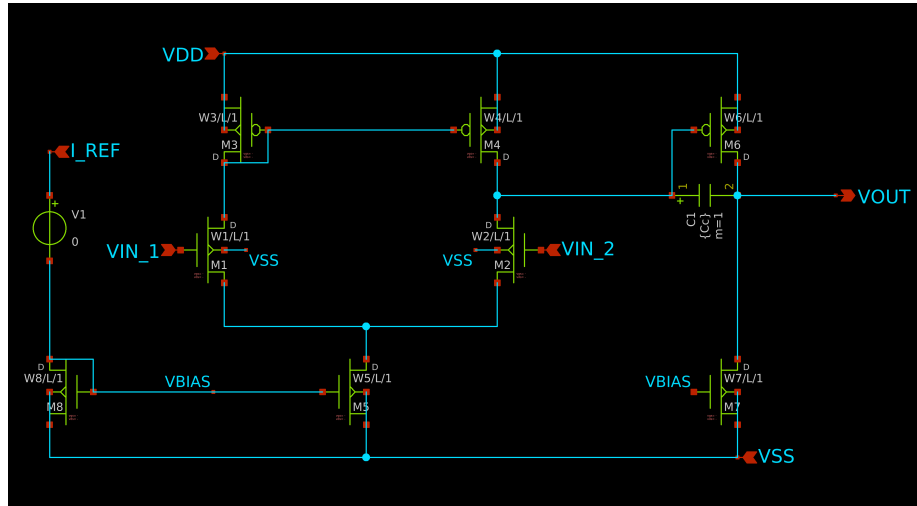


Figure 8: Final OTA Schematic

The final transistor sizing after all iterations is summarized in the table below:

Transistor	Type	W/L
M1, M2	NMOS	3.5
M3, M4	PMOS	10

Transistor	Type	W/L
M5	NMOS	3
M6	PMOS	86.6
M7	NMOS	13
M8	NMOS	3

Component values: $C_c = 2.5pF$, $C_L = 10pF$

4 Simulation Results

4.1 DC Operating Point

All transistors were verified to be in saturation before AC analysis. The testbench used is shown in Fig 9.

Transistor	$ V_{ov} $	$ V_{DS} $	Region
M1	0.745	1.748	Saturation
M2	0.745	1.706	Saturation
M3	0.216	1.116	Saturation
M4	0.216	1.159	Saturation
M5	0.463	2.134	Saturation
M6	0.259	1.320	Saturation
M7	0.463	3.679	Saturation
M8	0.463	1.263	Saturation

4.2 Open-Loop Gain (AC Analysis)

Simulation of measurement of open-loop gain of op-amp is a difficult step to perform. The reason is the high differential gain in op-amps.

In our case, with a gain of $5000V/V$, any offset voltage present is amplified by $5000.V_{OS}$ at the output. So, for any $V_{OS} < 0.5mV$, the output is driven to the maximum output swing possible, making it difficult to measure the open loop gain. This is shown in Fig 10.

To measure the open-loop gain, I have tried two different methods.

4.2.1 The LC Method

This is a conceptually neat method. A large inductor is used between the feedback between V_{out} and V_{IN1} , and a large capacitor is used between V_{IN1} and GND .

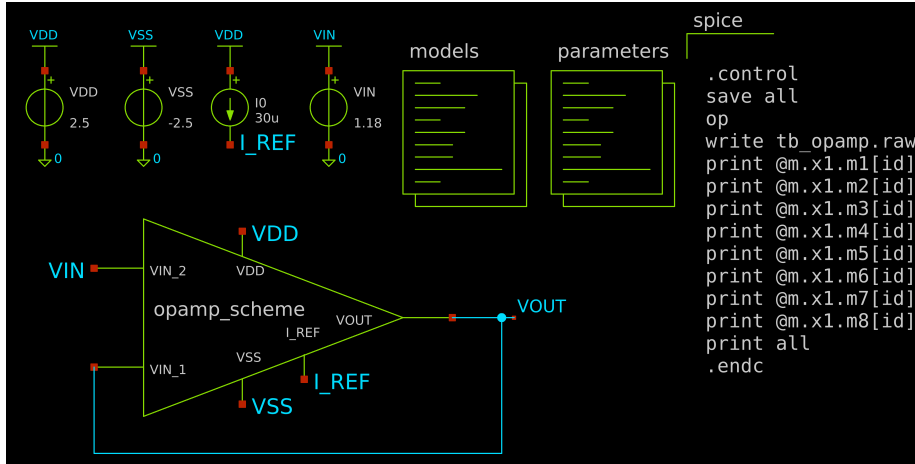


Figure 9: Testbench to verify operating points

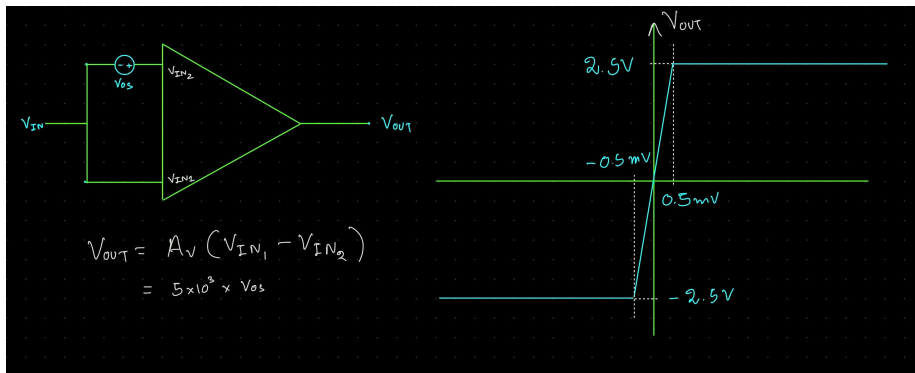


Figure 10: Open-Loop gain with offset voltage shown externally

At DC level, $f = 0$, so the inductor acts as a short circuit, while the capacitor acts as open circuit, this results in the amplifier working as a unity gain amplifier.

When a small AC signal (say, V_{in}) is applied, the inductor, which has a large value, essentially operates as an open circuit, while the capacitor acts as a short circuit to GND . So, $V_{out} = A_v \cdot V_{in}$.

The test bench and simulation results with this method are given in Fig 11 and Fig 12.

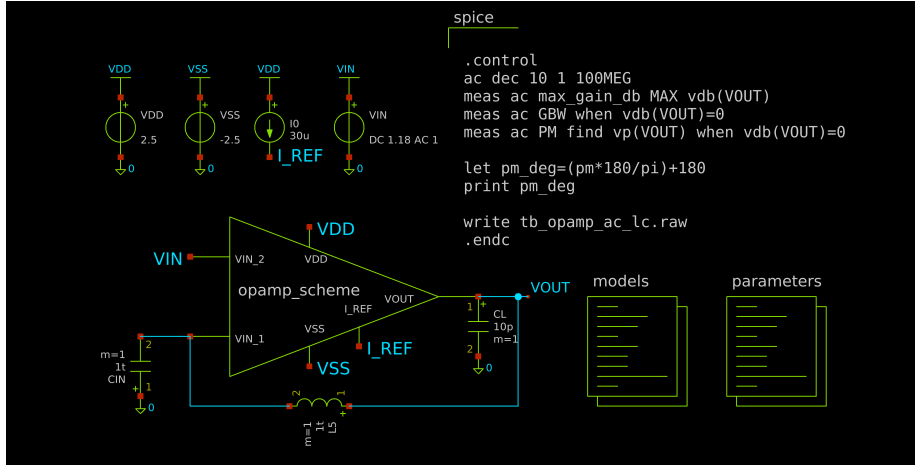


Figure 11: Test Bench for LC Method of measuring open-loop gain

However, this is not a practical method, since such large inductors and capacitors are generally not available.

4.2.2 The RC Method

This method uses a large resistor (R_f) in place of the inductor. Because the gate terminal of the input MOSFET has very high DC impedance, the steady-state current flowing through the feedback loop is approximately zero ($I_f \approx 0$). Consequently, there is zero voltage drop across R_f , this forces $V_{out} = V_{in1}$ and causes the circuit to operate as a unity-gain amplifier at DC.

On applying a small AC signal, the capacitor acts as a short-circuit to GND . So, again, operating in the open-loop configuration, $V_{out} = A_v \cdot V_{in}$.

In this circuit, it is necessary to select the $\frac{1}{RC}$ time constant a factor of $A_v(0)$ less than the anticipated dominant pole of the op-amp. The true open loop characteristics will not be observed until the frequency is approximately $\frac{A_v(0)}{RC}$. Above this frequency, the gain is essentially the open-loop gain of the op-amp. This method works well for both simulation and measurement.



Figure 12: Bode Plot for LC Method of measuring open-loop gain

4.2.2.1 Component Selection

To make sure the newly introduced zero doesn't interfere with our gain, values of $C_{in} = 10\mu F$ and $R_f = 10M\Omega$ were chosen so the pole lies very close to the origin.

$$f_z = \frac{1}{2\pi RC} \approx 1.59mHz$$

As mentioned above, the true open loop characteristics will not be observed until the frequency is approximately $\frac{A_v(0)}{RC}$, i.e, the new pole.

$$f_{obs} = \frac{A_v(0)}{2\pi RC} \approx 8.9Hz$$

So, we begin seeing the open-loop gain near 10Hz.

The test bench and simulation results with this method are given in Fig 13 and Fig 14.

The results using both methods are given below:

Parameter	LC Method	RC Method	Specification
Max Gain	74.07 dB	74.00 dB	>73.98 dB
GBW	5.85 MHz	5.85 MHz	5 MHz
Phase Margin	63.18°	63.19°	>60°

4.3 Transient Response and Slew Rate

Slew Rate is the rate of change of output voltage with respect to time. A large-signal step input was applied to measure the slew rate. The test bench and

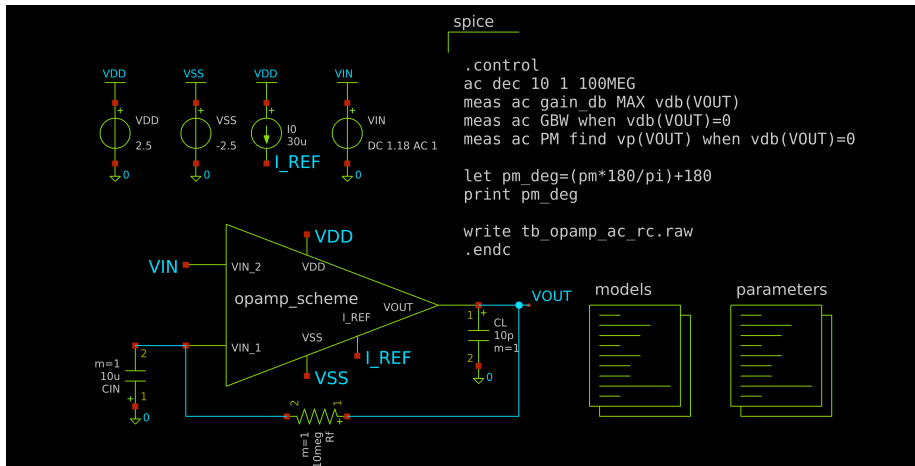


Figure 13: Test Bench for RC Method of measuring open-loop gain



Figure 14: Bode Plot for RC Method of measuring open-loop gain

output waveforms are shown in Fig 15 and Fig 16.

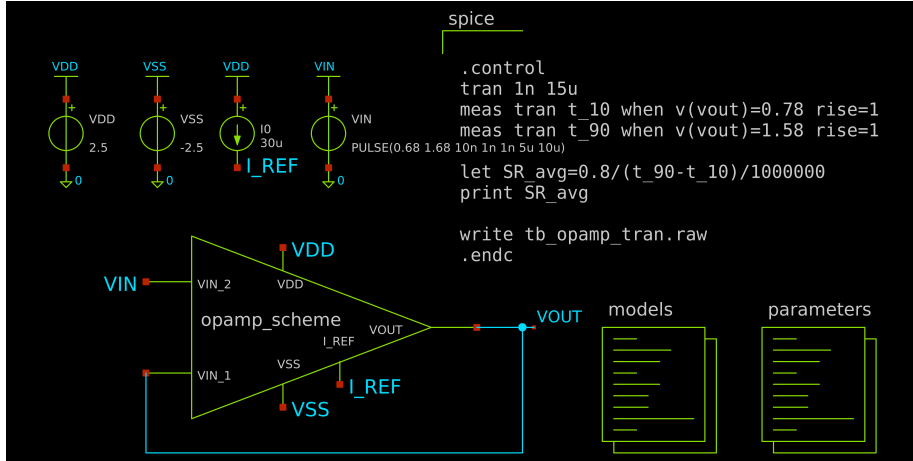


Figure 15: Test Bench to measure Slew Rate

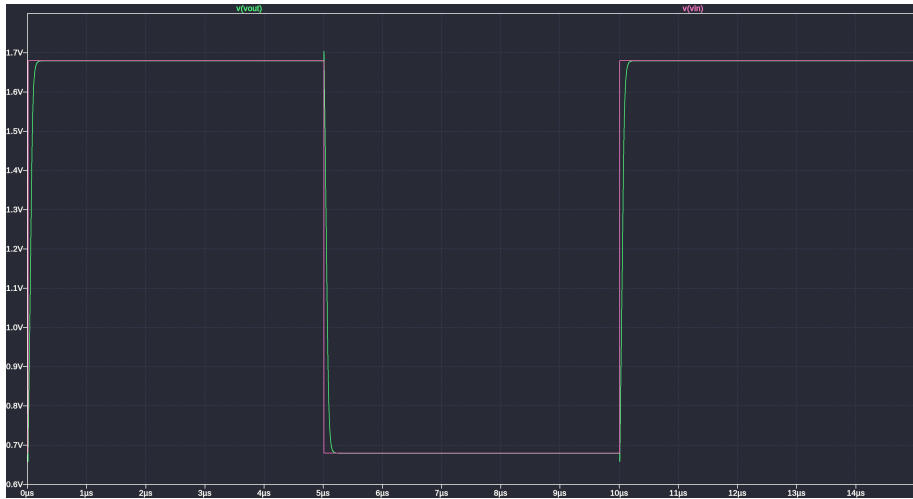


Figure 16: Time domain response of op-amp to measure Slew Rate

The average slew rate is measured between 10% and 90% of the final voltage swing. It is found to be:

$$SR = 10.637V/\mu s$$

4.4 DC Sweep - Linear Output Swing

The linear output swing is defined as the voltage range over which the amplifier maintains at least 90% of its ideal gain. Because the circuit is configured as

a unity-gain buffer, the ideal DC transfer characteristic has a slope of $1V/V$. Therefore, the absolute limits of the output swing are identified as the points where the derivative of the transfer curve $\frac{dV_{out}}{dV_{in}}$ drops below $0.9V/V$

The test bench and simulation result are given in Fig 17 and Fig 18.

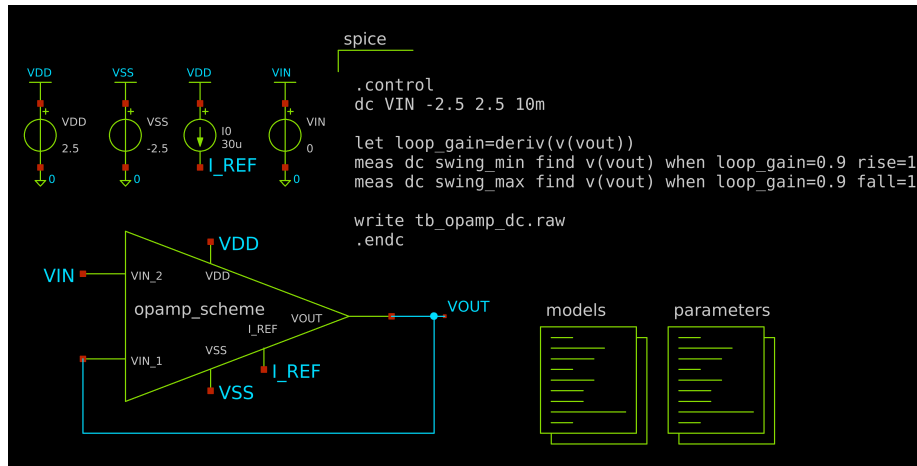


Figure 17: Test Bench to measure Linear Output Swing



Figure 18: Output Voltage response of input DC sweep.

The results obtained are given below:

- $V_{out}(max) = 2.44V$
- $V_{out}(min) = -2.27V$

5 Design Iterations

5.1 Iteration 1 - Initial Sizing ($\frac{W}{L} = 3$ for M1 and M2)

Parameter	Target	Result
Max Gain	$> 73.98dB$	$73.25dB$
GBW	$5MHz$	$4.55MHz$
Phase Margin	$> 60^\circ$	68.08°

Both Max Gain and GBW were not up to specification.

Since $GBW = \frac{g_{m1}}{2\pi C_c}$ and $g_{m1} = \sqrt{2K'_p \cdot \frac{W}{L} \cdot I_{D1}}$, increasing g_{m1} simultaneously increases both GBW as well as the first-stage gain.

So, increasing $\frac{W}{L}$ for M1 and M2 is the next logical step.

5.2 Iteration 2 - ($\frac{W}{L} = 3.5$ for M1 and M2)

Parameter	Target	Result
Max Gain	$> 73.98dB$	$74.07dB$
GBW	$5MHz$	$4.96MHz$
Phase Margin	$> 60^\circ$	66.20°
Slew Rate	$> 10V/\mu s$	$8.86V/\mu s$

While the gain and GBW seem to be well within specifications, the slew rate is lower than our target.

Since $SR = \frac{I_5}{C_c}$, we may either try increasing I_5 or decreasing C_c . Increasing I_5 requires us to go through every calculation step above again to get the updated sizing, so here we try decreasing C_c instead.

Our use of $C_c = 3pF$ is well above the condition of $C_c > 0.22C_L$, which means $C_c > 2.2pF$.

Let us use $C_c = 2.5pF$

5.3 Iteration 3 - ($C_c = 2.5pF$)

Parameter	Target	Result
Max Gain	$> 73.98dB$	$74.07dB$
GBW	$5MHz$	$5.85MHz$
Phase Margin	$> 60^\circ$	63.18°
Slew Rate	$> 10V/\mu s$	$10.64V/\mu s$

Now we seem to be within good margins of our specifications.

We will adopt this sizing.

6 Final Performance Summary

Parameter	Target	Result
Max Gain	$> 73.98dB$	$74.07dB$
GBW	$5MHz$	$5.85MHz$
Phase Margin	$> 60^\circ$	63.18°
Slew Rate	$> 10V/\mu s$	$10.64V/\mu s$
Power	$< 2mW$	$1.188mW$
Output Swing	$\pm 2V$	$-2.27to2.44V$

6.1 The Transistor and Component values used:


Transistor	Type	W/L	Current (μA)
M1, M2	NMOS	3.5	15.45, 15.48
M3, M4	PMOS	10	15.45, 15.48
M5	NMOS	3	30.93
M6	PMOS	86.6	176.68
M7	NMOS	13	176.68
M8	NMOS	3	30.00

Component values: $C_c = 2.5pF$, $C_L = 10pF$

7 Limitations and Known Critiques

The traditional Miller-compensated two-stage OTA with a compensation capacitor has known limitations. Baker notes that this topology, particularly with a zero-nulling resistor, has practical drawbacks—such as slower response times, larger layout areas, and higher power consumption—compared to more modern “indirect” compensation strategies, such as using split-length devices (Baker n.d.a).

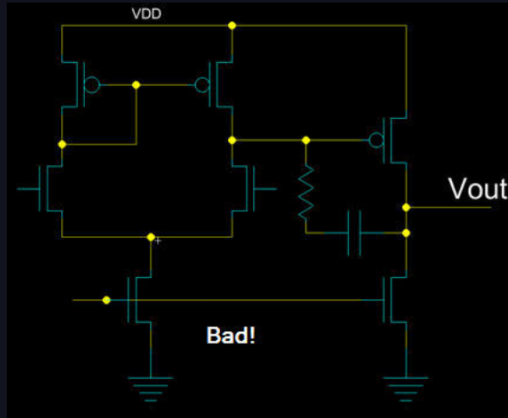Below is a simple two-stage op-amp using Miller compensation with a zero-nulling resistor. This is a bad design. Using this approach the op-amp is slower, larger, and (for a fixed speed requirement) burns more power.



A (much) better design uses split-length loads as seen below (Fig. 24.21). The RHP zero is removed and the compensation capacitor can be 4 to 10 times smaller (so the op-amp is faster!) Assuming the same widths for M3T/M3B and M4T/M4B they can be combined into a single MOSFET with the lengths of the devices summed (see problem 6.14 on page 160). For DC biasing purposes the topology above is exactly the same as the below topology.

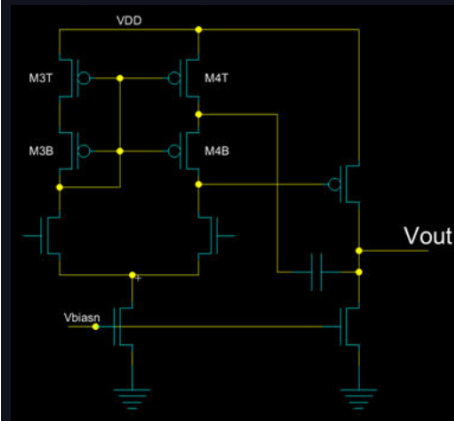


Figure 19: Baker's critique on traditional Miller compensation with a zero-nulling resistor. Adapted from (Baker n.d.a).

The goal of this project was to learn design methodology rather than implement a production-ready topology. The two-stage Miller-compensated OTA remains the standard introductory circuit for this purpose, providing clear insight into compensation theory, pole-zero placement, and the gain-bandwidth tradeoff. Exploring Baker’s recommended alternatives is a natural next step.

8 References

Allen, Phillip E., and Douglas R. Holberg. 2011. *CMOS Analog Circuit Design*. 3rd ed. Oxford University Press.

Baker, R. Jacob. n.d.a. *Bad Circuit Design 3 - Compensating an Op-Amp*. https://cmosedu.com/cmose1/bad_design/bad_design3/bad_design_3.htm.

Baker, R. Jacob. n.d.-b. *CMOSedu Level 3 SPICE Models*. https://cmosedu.com/cmose1/cmosedu_models.txt.

Kadam, M. 2021. “Dual Stage CMOS Operational Amplifier Design in Sky-Water 130nm Technology.” *2021 International Conference on Advances in Computing, Communication, and Control (ICAC3)*.

9 Personal Note

In this document, I have tried to include everything I have learnt designing this project as an absolute beginner to both SPICE as well as analog electronics in general.

I have spent nearly a month on this topic, out of which only about a week or two was spent on building this. I first discovered the two-stage CMOS OTA in an IEEE conference paper by M. Kadam(Kadam 2021), which used skywater pdk, I tried to understand it, but couldn’t get an intuitive feel for why the design choices were made the way they were.

But this motivated me to try to design this, since it seemed to use the basic building blocks I had already studied. I followed up with YouTube videos on the same topic, but again, while I was following the steps, I didn’t understand why we were making the choices that we were, but at the same time, I felt I was getting somewhat more comfortable with the topic.

I followed up with this question on Reddit and got incredibly helpful and detailed answers. Specifically, user u/Fast_Document1643 was very helpful, replied to all my questions with great patience, even if they were basic, and also pointed me towards the book I used as my main source of reference here: **CMOS Analog Circuit Design by Allen & Holberg**. The entire process of the design and the steps followed here are taken from the book.

I was also stuck in measuring the operating points and open loop gain for a long time, scratching my head because my op-amp would just stick to a value near the power supply. Like in every course, I have read that the offset voltage getting multiplied with a huge gain causes this, but I just couldn't think of that in my design process (I guess this is what experience develops?). After realizing this, work was a lot easier.

On the topic of other measurements, while I did know the concept of slew rate and output voltage swing, I didn't know how to measure their exact values, so I had to study up measurement techniques before actually using the `.dc` or `.tran` commands to find them.

For iterations, I had surprisingly little to worry about. Allen & Holberg's book mentioned the exact pitfalls and exactly which values to look into, so all I had to do was mess with them and look at parameters that were dependent on them and make sure all were within range. I probably should have rounded up the $\frac{W}{L}$ ratio of M6 to 87 instead of keeping it at 86.6, but I kinda forgot I didn't until everything was done, and when all the parameters seemed be within margin, I didn't really want to change anything.

Overall, even though I wanted to pull my hair out at times, I had fun building this. Coming from solving problems in my textbooks to actually designing something to meet specifications is a lot more challenging than I expected.